

---

# EXPERIMENT-1

## Objective: -

To Design and Implementation of Combinational Circuits (adder, decoder) in Gate Level

## Software Used: -

Cadence Incisive

## Theory: -

### Half Adder

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary number A and B. It is the basic building block for addition of two **single** bit numbers. This circuit has two outputs **carry** and **sum**.

### Decoder

A decoder is a combinational circuit. It has  $n$  input and to a maximum  $m = 2^n$  outputs. Decoder is identical to a demultiplexer without any data input. It performs operations which are exactly opposite to those of an encoder. Examples: - Code converters, BCD to seven segment decoders, Nixie tube decoders, Relay actuator.

## Half Adder Gate Level Modelling with Testbench: -

```
module half_adder(  
    input i0,  
    input i1,  
    output s,  
    output c  
);  
    and(c,i0,i1);  
    xor(s,i0,i1);  
endmodule
```

### Testbench: -

initial begin

```
// Initialize Inputs
```

```
i0 = 0;
```

```
i1 = 0;
```

```
// Wait 100 ns for global reset to finish
```

```
#100;
```

```
// Add stimulus here
```


```
#100; i0 = 0; i1 = 1;
```

```
#100; i0 = 1; i1 = 0;
```

```
#100; i0 = 1; i1 = 1;
```

end

### Output: -

 

### Decoder Gate Level Modelling with Testbench: -

```
module decoder24_gate(en,a,b,y);
```

```
// declare input and output ports
```

```
input en,a,b;
```

```
output [3:0]y;
```

---

```

// supportive connections required
// to connect nand gates
wire enb,na,nb;
// instantiate 4 nand gates and 3 not gates
// make connections by referring the above logic diagram
not n0(enb,en);
not n1(na,a);
not n2(nb,b);
nand n3(y[0],enb,na,nb);
nand n4(y[1],enb,na,b);
nand n5(y[2],enb,a,nb);
nand n6(y[3],enb,a,b);
endmodule

```

### **Testbench: -**

```

module tb;
// input port are declared in reg(register)
reg a,b,en;
// output port are declared in wire(net)
wire [3:0]y;
// instantiate design block
decoder24_gate dut(en,a,b,y);
initial
begin
$monitor("en=%b a=%b b=%b y=%b",en,a,b,y);
// with reference to truth table provide input values


```

```

en=1;a=1'bx;b=1'bx;#5
en=0;a=0;b=0;#5
en=0;a=0;b=1;#5
en=0;a=1;b=0;#5
en=0;a=1;b=1;#5
// terminate simulation using $finish system task
$finish;
end
endmodule

```

### Output: -

 

---

# EXPERIMENT-2

## Objective: -

To Design and Implementation of Multiplexer and Comparator circuits in data-flow level

## Software Used: -

Cadence Incisive

## Theory: -

### Multiplexer

A multiplexer is a device that selects one output from multiple inputs. It is also known as a data selector. We refer to a multiplexer with the terms *MUX* and *MPX*. Multiplexers are used in communication systems to increase the amount of data sent over a network within a certain amount of time and bandwidth. It allows us to squeeze multiple data lines into one data line. It switches between one of the many input lines and combines them one by one to the output. It decides which input line to switch using a control signal.

### Comparator

A decoder is a combinational circuit. It has  $n$  input and to a maximum  $m = 2^n$  outputs. Decoder is identical to a demultiplexer without any data input. It performs operations which are exactly opposite to those of an encoder. Examples: - Code converters, BCD to seven segment decoders, Nixie tube decoders, Relay actuator.

## Multiplexer Data Flow Level Modelling with Testbench: -

```
module mux2X1 (in0,in1,sel,out);
```

```
input in0, in1, sel;
```

```
output out;
```


---

```
assign out=(sel)?in1:in0;  
endmodule
```

### Testbench: -

```
module mux2X1_tb;  
reg in0, in1;  
reg sel;  
wire out;  
mux2X1 uut(.in0(in0), .in1(in1), .sel(sel), .out(out));  
initial begin  
    $monitor( "in0=%d, in1=%d, sel= %d, out=%d", in0,in1,sel,out);  
    for (int i=0; i<8; i=i+1) begin  
        {in0,in1,sel} = i;  
        #10;  
    end  
end  
endmodule
```

### Output: -

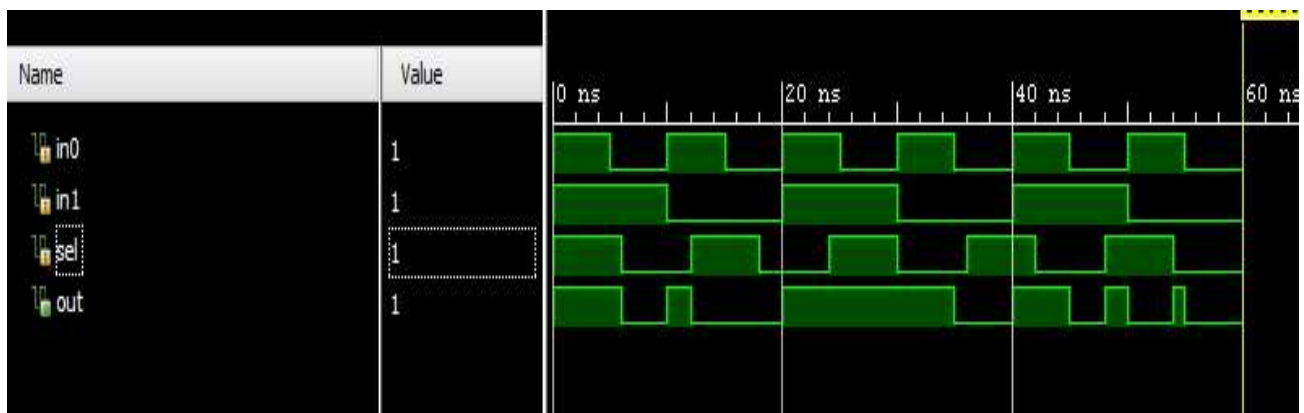

---

## Comparator Data Flow Level Modelling with Testbench: -

```
// Verilog code for 2-bit comparator
module comparator(input [1:0] A,B, output A_less_B, A_equal_B,
A_greater_B);
wire tmp1,tmp2,tmp3,tmp4,tmp5, tmp6, tmp7, tmp8;
// A = B output
xnor u1(tmp1,A[1],B[1]);
xnor u2(tmp2,A[0],B[0]);
and u3(A_equal_B,tmp1,tmp2);
// A less than B output
assign tmp3 = (~A[0])& (~A[1])& B[0];
assign tmp4 = (~A[1])& B[1];
assign tmp5 = (~A[0])& B[1]& B[0];
assign A_less_B = tmp3 | tmp4 | tmp5;
// A greater than B output
assign tmp6 = (~B[0])& (~B[1])& A[0];
assign tmp7 = (~B[1])& A[1];
assign tmp8 = (~B[0])& A[1]& A[0];
assign A_greater_B = tmp6 | tmp7 | tmp8;
endmodule
`timescale 10 ps/ 10 ps
```

## Testbench: -

```
module tb_comparator;
reg [1:0] A, B;
wire A_less_B, A_equal_B, A_greater_B;
integer i;
// device under test
comparator dut(A,B,A_less_B, A_equal_B, A_greater_B);
initial begin
    for (i=0;i<4;i=i+1)
        begin
            A = i;
```

```

        B = i + 1;
        #20;
    end
    for (i=0;i<4;i=i+1)
    begin
        A = i;
        B = i;
        #20;
    end
    for (i=0;i<4;i=i+1)
    begin
        A = i+1;
        B = i;
        #20;
    end
end
endmodule

```

**Output: -**





---

# EXPERIMENT-3

## Objective: -

To Implement multiplexer, decoder in Behavioural Level

## Software Used: -

Cadence Incisive

## Theory: -

### Multiplexer

A multiplexer is a device that selects one output from multiple inputs. It is also known as a data selector. We refer to a multiplexer with the terms *MUX* and *MPX*. Multiplexers are used in communication systems to increase the amount of data sent over a network within a certain amount of time and bandwidth. It allows us to squeeze multiple data lines into one data line. It switches between one of the many input lines and combines them one by one to the output. It decides which input line to switch using a control signal.

### Decoder

A decoder is a combinational circuit. It has  $n$  input and to a maximum  $m = 2^n$  outputs. Decoder is identical to a demultiplexer without any data input. It performs operations which are exactly opposite to those of an encoder. Examples: - Code converters, BCD to seven segment decoders, Nixie tube decoders, Relay actuator.

### Multiplexer Behavioural Level Modelling with Testbench: -

```
module m41 ( a, b, c, d, s0, s1, out);  
input wire a, b, c, d;  
input wire s0, s1;  
output reg out;
```

---

```
always @ (a or b or c or d or s0, s1)
```

```
begin
```

```
case (s0 | s1)
```

```
2'b00 : out <= a;
```

```
2'b01 : out <= b;
```

```
2'b10 : out <= c;
```

```
2'b11 : out <= d;
```

```
endcase
```

```
end
```

```
endmodule
```

**Testbench: -**

```
module top;
```

```
wire out;
```

```
reg a;
```

```
reg b;
```

```
reg c;
```

```
reg d;
```

```
reg s0, s1;
```

```
m41 name(.out(out), .a(a), .b(b), .c(c), .d(d), .s0(s0), .s1(s1));
```

```
initial
```

```
begin
```

```
a=1'b0; b=1'b0; c=1'b0; d=1'b0;
```

```
s0=1'b0; s1=1'b0;
```

```
#500 $finish;
```

```
end
```

```
always #40 a=~a;
```


```
always #20 b=~b;
```

```

always #10 c=~c;
always #5 d=~d;
always #80 s0=~s0;
always #160 s1=~s1;
always@(a or b or c or d or s0 or s1)
$monitor("At time = %t, Output = %d", $time, out);
endmodule;

```

**Output: -**

 

**Decoder Behavioural Level Modelling with Testbench: -**

```

module 2_4_DEC( input [1:0]din, output [3:0]dout );
reg [3:0]dout;
always @(din)
case (din)
0 : dout[0] = 1;
1 : dout[1] = 1;
2 : dout[2] = 1;
3 : dout[3] = 1;
default : dout = 4'bxxxx;
endcase
endmodule

```

### Testbench: -

```
initial begin
// Initialize Inputs
din = 0;
// Wait 100 ns for global reset to finish
#100;
// Add stimulus here
#100; din=0;
#100; din=1;
#100; din=2;
#100; din=3;
end
initial begin
#100
$monitor("din=%b, dout=%b", din, dout);
end
endmodule
```

### Output: -

Name	Value	0 ns	200 ns	400 ns	600 ns
dout[3:0]	1000	0001	0010	0100	1000
din[1:0]	11	00	01	10	11

---

# EXPERIMENT- 4

## Objective: -

To Design and Implementation of ALU

## Software Used: -

Cadence Incisive

## Theory: -

### ALU

An arithmetic logic unit (ALU) is a digital circuit used to perform arithmetic and logic operations. It represents the fundamental building block of the central processing unit (CPU) of a computer. Modern CPUs contain very powerful and complex ALUs. In addition to ALUs, modern CPUs contain a control unit (CU). Most of the operations of a CPU are performed by one or more ALUs, which load data from input registers. A register is a small amount of storage available as part of a CPU. The control unit tells the ALU what operation to perform on that data, and the ALU stores the result in an output register. The control unit moves the data between these registers, the ALU, and memory.

## Multiplexer Behavioural Level Modelling with Testbench: -

```
module alu(  
    input [7:0] A,B, // ALU 8-bit Inputs  
    input [3:0] ALU_Sel,// ALU Selection  
    output [7:0] ALU_Out, // ALU 8-bit Output  
    output CarryOut // Carry Out Flag  
);  
    reg [7:0] ALU_Result;  
    wire [8:0] tmp;  
    assign ALU_Out = ALU_Result; // ALU out  
    assign tmp = {1'b0,A} + {1'b0,B};  
    assign CarryOut = tmp[8]; // Carryout flag
```

---

```

always @(*)
begin
    case(ALU_Sel)
    4'b0000: // Addition
        ALU_Result = A + B ;
    4'b0001: // Subtraction
        ALU_Result = A - B ;
    4'b0010: // Multiplication
        ALU_Result = A * B;
    4'b0011: // Division
        ALU_Result = A/B;
    4'b0100: // Logical shift left
        ALU_Result = A<<1;
    4'b0101: // Logical shift right
        ALU_Result = A>>1;
    4'b0110: // Rotate left
        ALU_Result = {A[6:0],A[7]};
    4'b0111: // Rotate right
        ALU_Result = {A[0],A[7:1]};
    4'b1000: // Logical and
        ALU_Result = A & B;
    4'b1001: // Logical or
        ALU_Result = A | B;
    4'b1010: // Logical xor
        ALU_Result = A ^ B;
    4'b1011: // Logical nor
        ALU_Result = ~(A | B);
    4'b1100: // Logical nand
        ALU_Result = ~(A & B);
    4'b1101: // Logical xnor
        ALU_Result = ~(A ^ B);
    4'b1110: // Greater comparison
        ALU_Result = (A>B)?8'd1:8'd0 ;
    4'b1111: // Equal comparison
        ALU_Result = (A==B)?8'd1:8'd0 ;
    default: ALU_Result = A + B ;
end

```

---

```
        endcase
    end
```

```
endmodule
```

### **Testbench: -**

```
`timescale 1ns / 1ps
```

```
module tb_alu;
//Inputs
reg[7:0] A,B;
reg[3:0] ALU_Sel;


//Outputs
wire[7:0] ALU_Out;
wire CarryOut;
// Verilog code for ALU
integer i;
alu test_unit(
    A,B, // ALU 8-bit Inputs
    ALU_Sel,// ALU Selection
    ALU_Out, // ALU 8-bit Output
    CarryOut // Carry Out Flag
);
initial begin
// hold reset state for 100 ns.
    A = 8'h0A;
    B = 4'h02;
    ALU_Sel = 4'h0;
    for (i=0;i<=15;i=i+1)
    begin
        ALU_Sel = ALU_Sel + 8'h01;
        #10;
    end;
end;
```

```

    A = 8'hF6;
    B = 8'h0A;
end
endmodule

```

**Output: -**

 



---

# EXPERIMENT- 5

## Objective: -

To Implement D-FF and JK FF in behavioral level

## Software Used: -

Cadence Incisive

## Theory: -

A flip flop can store one bit of data. Hence, it is known as a memory cell. Flip-flops are synchronous circuits since they use a clock signal. Using flip flops, we build complex circuits such as RAMs, Shift Registers, etc.

A D flip-flop stands for data or delay flip-flop. The outputs of this flip-flop are equal to the inputs.

The J-K flip-flop is the most versatile of the basic flip flops. The JK flip flop is a gated SR flip-flop with the addition of a clock input circuitry that prevents the illegal or invalid output condition that can occur when both inputs S and R are equal to logic 1. Due to this additional clocked input, a JK flip-flop has four possible input combinations, “logic 1”, “logic 0”, “no change” and “toggle”.

## D Flip Flop Behavioral Level Modelling with Testbench: -

```
module dff_behavioral(d,clk,clear,q,qbar); // Synchronous
input d, clk, clear;
output reg q, qbar;
always@(posedge clk)
begin
if(clear== 1)
q <= 0;
qbar <= 1;
```

---

```

else
q <= d;
qbar = !d;
end
endmodule

module dff_behavioral(d,clk,clear,q,qbar); // Asynchronous
input d, clk, clear;
output reg q, qbar;
always@(posedge clk or posedge clear)
begin
if(clear== 1)
q <= 0;
qbar <= 1;
else
q <= d;
qbar = !d;
end
endmodule

```

**Testbench: -**

```

module dff_test;
reg D, CLK,reset;
wire Q, QBAR;
dff_behavior dut(.q(Q), .qbar(QBAR), .clear(reset), .d(D), .clk(CLK)); //
instantiation by port name.

$monitor("simtime = %g, CLK = %b, D = %b,reset = %b, Q = %b, QBAR =
%b", $time, CLK, D, reset, Q, QBAR);
initial begin
    clk=0;

```


```

    forever #10 clk = ~clk;
end
initial begin
    reset=1; D <= 0;
    #100; reset=0; D <= 1;
    #100; D <= 0;
    #100; D <= 1;
end
endmodule


```

**Output: -**

### D Flip Flop (Synchronous)

 

### D Flip Flop (Asynchronous)

 

### JK Flip Flop Behavioral Level Modelling with Testbench: -

```

module jkff_behave(clk,j,knq,qbar);
input clk,j,k;
output reg q,qbar;
always@(posedge clk)

```

---

```
begin
if(k = 0)
begin
q <= 0;
qbar <= 1;
end
always@(posedge clk)
begin
if(k = 0)
begin
q <= 0;
qbar <= 1;
end
else if(j = 1)
begin
q <= 0;
qbar <= 0;
end
else if(j = 0 & k = 0)
begin
q <= q;
qbar <= qbar;
end
else if(j = 1 & k = 1)
begin
q <= ~q;
qbar <= ~qbar;
```


```

    end
end
endmodule

Testbench: -
module jkff_test;
reg J,K, CLK;
wire Q, QBAR;
jkff_behavior dut(.q(Q), .qbar(QBAR), .j(J), .k(K), .clk(CLK));
$monitor("simtime = %g, CLK = %b, J = %b, K = %b, Q = %b, QBAR = %b", $time, CLK, J, K, Q, QBAR);
initial begin
    clk=0;
    forever #10 clk = ~clk;
end
initial begin
    J= 1; K= 0;
    #100; J= 0; K= 1;
    #100; J= 0; K= 0;
    #100; J= 1; K=1;
end
endmodule

```

**Output: -**

 

---

# EXPERIMENT- 6

## Objective: -

To Design and Implementation of Shift Register

## Software Used: -

Cadence Incisive

## Theory: -

In digital electronics, a shift register is a cascade of flip-flops where the output pin q of one flop is connected to the data input pin (d) of the next. Because all flops work on the same clock, the bit array stored in the shift register will shift by one position. For example, if a 5-bit right shift register has an initial value of 10110 and the input to the shift register is tied to 0, then the next pattern will be 01011 and the next 00101.

## Shift Register Modelling with Testbench: -

```
module free_run_shift_reg
    #(parameter N=8)
    (
        input wire clk, reset,
        input wire s_in,
        output wire s_out
    );
    reg [N-1:0] r_reg;
    wire [N-1:0] r_next;
    always @(posedge clk, negedge reset)
    begin
        if (~reset)
            r_reg <= 0;
```

---

```
    else
        r_reg <= r_next;
    end
    assign r_next = {s_in, r_reg[N-1:1]};
    assign s_out = r_reg[0];
endmodule
```

### **Testbench: -**

```
`timescale 1ns / 1ps
module stimulus;
    // Inputs
    reg clk ;
    reg reset;
    // Outputs
    reg s_in;
    wire s_out;
    // Instantiate the Unit Under Test (UUT)
    free_run_shift_reg #(2) s1 (
        .clk(clk),
        .reset(reset),
        .s_in(s_in),
        .s_out(s_out)
    );

    integer i, j;
    initial
    begin
```

---

```
clk = 0;
for(i =0; i<=40; i=i+1)
begin
    #10 clk = ~clk;
end
end
```

```
initial
begin
```

```
$dumpfile("test.vcd");
$dumpvars(0,stimulus);
```

```
s_in = 0; reset =1;
#2 s_in = 0 ; reset = 0;
#2 reset =1;
for(i =0; i<=10; i=i+1)
begin
    #20 s_in = ~s_in;
end
#20 s_in =1;
#20 s_in = 1;
#20 s_in =0;
#20 s_in =1;
#20 s_in = 1;
#20 s_in =0;
```



```

#20 s_in =1;
#20 s_in = 1;
#20 s_in =0;
end

```


```

initial begin
    $monitor("clk=%d s_in=%d,s_out=%d",clk,s_in, s_out);
end

```

```
endmodule
```

## Output: -

 

---

# EXPERIMENT- 7

## Objective: -

To Design and Implementation of Asynchronous Counter.

## Software Used: -

Cadence Incisive

## Theory: -

Asynchronous counters are those whose output is free from the clock signal. Because the flip flops in asynchronous counters are supplied with different clock signals, there may be delay in producing output. The required number of logic gates to design asynchronous counters is very less. So they are simple in design.

## Asynchronous Counter with Testbench: -

```
module counter ( input clk, input rstn, output reg[3:0] out);  
always @(posedge clk) begin  
    if (! rstn)  
        out <= 0;  
    else  
        out <= out + 1;  
    end  
endmodule
```

## Testbench: -


```
module tb_counter; reg clk; reg rstn; wire [3:0] out;  
counter c0 ( .clk (clk), .rstn (rstn), .out (out));  
always #5 clk = ~clk;  
initial begin  
    clk <= 0;  
    rstn <= 0;
```

```

#20 rstn <= 1;
#80 rstn <= 0;
#50 rstn <= 1;
#20 $finish;
end
endmodule

```

## Output:-

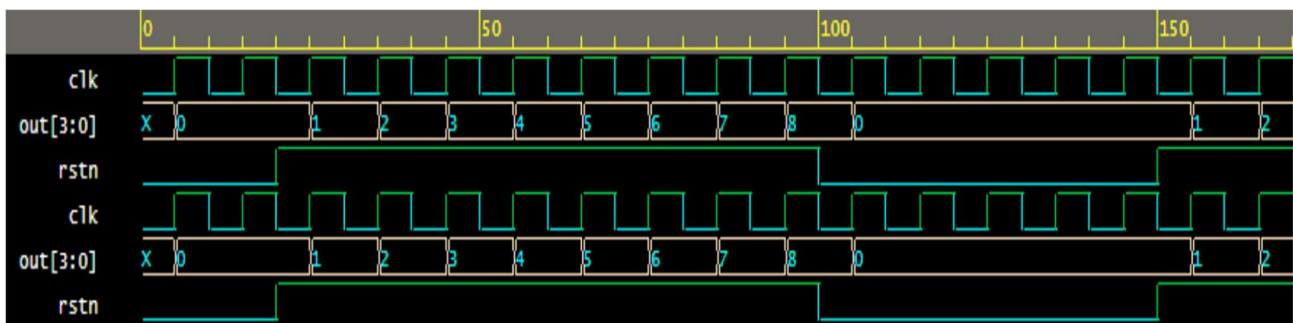

---

# EXPERIMENT- 8

## Objective: -

To Design and Implementation of Synchronous Counter.

## Software Used: -

Cadence Incisive

## Theory: -

The synchronous counter also referred to as a parallel counter is the one in which each establishing flip flops are clocked with the similar clock input at the same time. In the synchronous counter, all the flip-flops in the cascade network are independently linked to an external clock.

## Synchronous Counter with Testbench: -

```
module synchronouscounter(clk,reset,count);  
    input clk,reset;  
    output reg [3:0] count;  
    always@(posedge clk)  
    begin  
        if(reset)  
            count <= 4'b0000;  
        else  
            count <= count + 1;  
        end  
    endmodule
```

## Testbench: -


```
module synchronouscountertb;  
    reg clk, reset;  
    wire [3:0] count;  
    synchronouscounter syncctr(clk,reset,count);  
endmodule
```

```

initial
begin
    clk = 0;
    reset = 1;
    #125
    reset = 0;
    #4500;
    $finish;
end
always #50 clk=~clk;
always@(posedge clk)
begin
    $display ("value is %d", count);
end
endmodule

```

**Output: -**

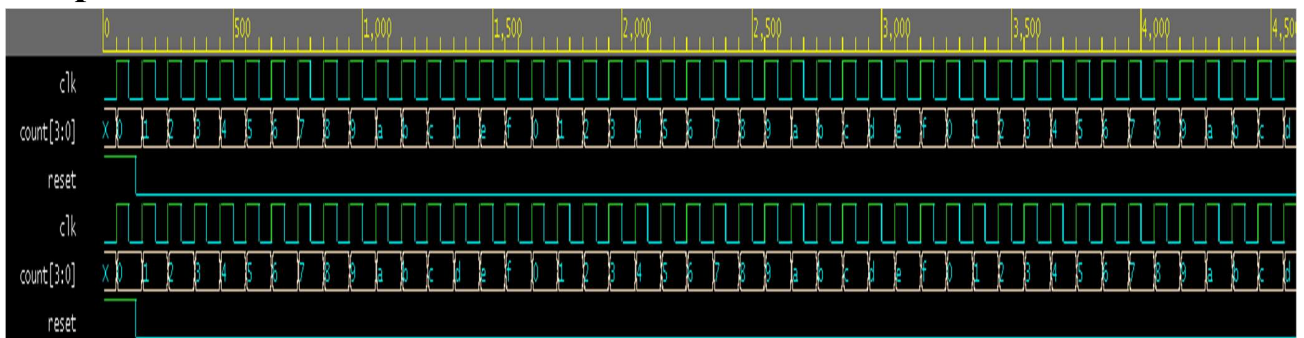

---

# EXPERIMENT- 9

## Objective: -

To Design and Implementation of Sequence Detector in FSM.

## Software Used: -

Cadence Incisive

## Theory: -

A sequence detector is a sequential circuit that outputs 1 when a particular pattern of bits sequentially arrives at its data input. The figure below shows a block diagram of a sequence detector. It has two inputs and one output.

## Sequence Detector Verilog code with Testbench: -

```
module det_1011 ( input clk,
                  input rstn,
                  input in,
                  output out );

    parameter IDLE    = 0,
                S1     = 1,
                S10    = 2,
                S101    = 3,
                S1011   = 4;

    reg [2:0] cur_state, next_state;

    assign out = cur_state == S1011 ? 1 : 0;

    always @ (posedge clk) begin
        if (!rstn)
```

---

```
        cur_state <= IDLE;
    else
        cur_state <= next_state;
    end

always @(cur_state or in) begin
    case (cur_state)
        IDLE : begin
            if (in) next_state = S1;
            else next_state = IDLE;
        end

        S1: begin
`ifdef BUG_FIX
            if (in) next_state = S1;
`else
            if (in) next_state = IDLE;
`endif
        else next_state = S10;
    end

    S10 : begin
        if (in) next_state = S101;
        else next_state = IDLE;
    end

    S101 : begin
        if (in) next_state = S1011;
`ifdef BUG_FIX
            else next_state = S10;
`else
```

---

```

        else next_state = IDLE;
    `endif
end

S1011: begin
    next_state = IDLE;
end
endcase
end
endmodule

```

### **Testbench: -**

```

module tb;
    reg          clk, in, rstn;
    wire          out;
    reg [1:0] l_dly;
    reg          tb_in;
    integer  loop = 20;

    always #10 clk = ~clk;

    det_1011 u0 ( .clk(clk), .rstn(rstn), .in(in), .out(out) );

    initial begin
        clk <= 0;
        rstn <= 0;
        in <= 0;

        repeat (5) @ (posedge clk);
        rstn <= 1;
    end
endmodule

```



---

```

`ifndef RANDOM
    // Generate a directed pattern
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 0;
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 0;
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 0;
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 0;
    @(posedge clk) in <= 1;
    @(posedge clk) in <= 1;

`else
    // Or random stimulus using a for loop that drives a random
    // value of input N times, but there is lesser chance to hit
    // this pattern
    for (int i = 0 ; i < loop; i ++) begin
        l_dly = $random;
        repeat (l_dly) @ (posedge clk);
        tb_in = $random;
        in <= tb_in;
    end
`endif

    #100 $finish;
end

always @ (posedge clk) begin
    $strobe ("T=%0t in=%0b out=%0b", $time, in, out);

```

```
end
endmodule
```

Output: -



---

# EXPERIMENT- 10

## Objective: -

To Design and Implementation of Traffic Light Signal System in FSM.

## Software Used: -

Cadence Incisive

## Theory: -

Traffic light simulation is a classic text book problem used to demonstrate a finite state machine. A FSM is a system with finite states, finite inputs, finite outputs. It has a known number of states, inputs, and outputs.

## Traffic Light Signal Verilog code with Testbench: -

```
module traffic_light(light_highway, light_farm, C, clk, rst_n);
parameter HGRE_FRED=2'b00, // Highway green and farm red
    HYEL_FRED = 2'b01, // Highway yellow and farm red
    HRED_FGRE=2'b10, // Highway red and farm green
    HRED_FYEL=2'b11; // Highway red and farm yellow
input C, // sensor
    clk, // clock = 50 MHz
    rst_n; // reset active low
output reg[2:0] light_highway, light_farm; // output of lights
// fpga4student.com FPGA projects, VHDL projects, Verilog projects
reg[27:0] count=0, count_delay=0;
reg delay10s=0,
    delay3s1=0, delay3s2=0, RED_count_en=0, YELLOW_count_en1=0, YELLO
    W_count_en2=0;
wire clk_enable; // clock enable signal for 1s
```

---

```

reg[1:0] state, next_state;
// next state
always @(posedge clk or negedge rst_n)
begin
if(~rst_n)
state <= 2'b00;
else
state <= next_state;
end
// FSM
always @(*)
begin
case(state)
HGRE_FRED: begin // Green on highway and red on farm way
RED_count_en=0;
YELLOW_count_en1=0;
YELLOW_count_en2=0;
light_highway = 3'b001;
light_farm = 3'b100;
if(C) next_state = HYEL_FRED;
// if sensor detects vehicles on farm road,
// turn highway to yellow -> green
else next_state =HGRE_FRED;
end
HYEL_FRED: begin// yellow on highway and red on farm way
light_highway = 3'b010;
light_farm = 3'b100;

```

---

```

    RED_count_en=0;
    YELLOW_count_en1=1;
    YELLOW_count_en2=0;
    if(delay3s1) next_state = HRED_FGRE;
    // yellow for 3s, then red
    else next_state = HYEL_FRED;
end
HRED_FGRE: begin// red on highway and green on farm way
    light_highway = 3'b100;
    light_farm = 3'b001;
    RED_count_en=1;
    YELLOW_count_en1=0;
    YELLOW_count_en2=0;
    if(delay10s) next_state = HRED_FYEL;
    // red in 10s then turn to yello -> green again for high way
    else next_state =HRED_FGRE;
end
HRED_FYEL:begin// red on highway and yellow on farm way
    light_highway = 3'b100;
    light_farm = 3'b010;
    RED_count_en=0;
    YELLOW_count_en1=0;
    YELLOW_count_en2=1;
    if(delay3s2) next_state = HGRE_FRED;
    // turn green for highway, red for farm road
    else next_state =HRED_FYEL;
end

```

---

```
default: next_state = HGRE_FRED;
endcase
end
// fpga4student.com FPGA projects, VHDL projects, Verilog projects
// create red and yellow delay counts
always @(posedge clk)
begin
if(clk_enable==1) begin
if(RED_count_en||YELLOW_count_en1||YELLOW_count_en2)
count_delay <=count_delay + 1;
if((count_delay == 9)&&RED_count_en)
begin
delay10s=1;
delay3s1=0;
delay3s2=0;
count_delay<=0;
end
else if((count_delay == 2)&&YELLOW_count_en1)
begin
delay10s=0;
delay3s1=1;
delay3s2=0;
count_delay<=0;
end
else if((count_delay == 2)&&YELLOW_count_en2)
begin
delay10s=0;
```

---

```

    delay3s1=0;
    delay3s2=1;
    count_delay<=0;
end
else
begin
    delay10s=0;
    delay3s1=0;
    delay3s2=0;
end
end
end
// create 1s clock enable
always @(posedge clk)
begin
    count <=count + 1;
    //if(count == 50000000) // 50,000,000 for 50 MHz clock running on real
FPGA
    if(count == 3) // for testbench
        count <= 0;
end
    assign clk_enable = count==3 ? 1: 0; // 50,000,000 for 50MHz running on
FPGA
endmodule

```

### **Testbench: -**

```

`timescale 10 ns/ 1 ps
// 2. Preprocessor Directives

```

---

```

`define DELAY 1
// 3. Include Statements
`include "counter_define.h"
module tb_traffic;
// 4. Parameter definitions
parameter ENDTIME = 400000;
// 5. DUT Input regs
//integer count, count1, a;
reg clk;
reg rst_n;
reg sensor;
wire [2:0] light_farm;
// 6. DUT Output wires
wire [2:0] light_highway;

// fpga4student.com FPGA projects, VHDL projects, Verilog projects
// 7. DUT Instantiation
traffic_light tb(light_highway, light_farm, sensor, clk, rst_n);

// 8. Initial Conditions
initial
begin
    clk = 1'b0;
    rst_n = 1'b0;
    sensor = 1'b0;
    // count = 0;
    /// count1=0;
    // a=0;
end
// 9. Generating Test Vectors
initial

```



---

```
begin
main;
end
task main;
fork
clock_gen;
reset_gen;
operation_flow;
debug_output;
endsimulation;
join
endtask
task clock_gen;
begin
forever #`DELAY clk = !clk;
end
endtask
task reset_gen;
begin
rst_n = 0;
# 20
rst_n = 1;
end
endtask
// fpga4student.com FPGA projects, VHDL projects, Verilog projects
task operation_flow;
begin
sensor = 0;
# 600
sensor = 1;
# 1200
```

---

```

sensor = 0;
# 1200
sensor = 1;
end
endtask
// 10. Debug output
task debug_output;
begin
$display("-----");
    $display("-----");
$display("----- SIMULATION RESULT -----");
$display("-----");
$display("-----");
$display("-----");
$monitor("TIME = %d, reset = %b, sensor = %b, light of highway = %h,
light of farm road = %h",$time,rst_n ,sensor,light_highway,light_farm );
end
endtask
// fpga4student.com FPGA projects, VHDL projects, Verilog projects
//12. Determines the simulation limit
task endsimulation;
begin
#ENDTIME
$display("----- THE SIMUALTION END -----");
$finish;
end
endtask
endmodule

```

Output: -

